Code No.: 20493 E

Sub. Code: CSCS 31

B.Sc. (CBCS) DEGREE EXAMINATION, NOVEMBER 2023.

Third Semester

Computer Science

Skill Based Subject - DIGITAL DESIGN

(For those who joined in July 2021-2022)

Time: Three hours

Maximum: 75 marks

PART A — $(10 \times 1 = 10 \text{ marks})$

Answer ALL questions.

Choose the correct answer:

- 1. What is the decimal equivalent of 0.11012?
 - (a) 0.78125
- (b) 0.8125
- (c) 0.9375
- (d) 0.6875
- 2. Which code is used in IBM make devices?
 - (a) BCD
- (b) GRAY code
- (c) ASC II
- (d) EBCDIC

- $3. \quad AB + \overline{A}C + BC = ---$
 - (a) $(A + B)(\overline{A} + C)$
- (b) $AB + \overline{A}C$
- (e) AB + BC
- (d) $\overline{A}C + BC$
- 4. How many fundamental products are there for three variables?
 - (a) 2
- (b) 3
- (c) 4
- (d) 8
- 5. A ⊕ B = ____
 - (a) A + B
- (b) $AB + \overline{A}\overline{B}$
- (c) $A\overline{B} + \overline{A}B$
- (d) $\overline{A} + \overline{B}$
- 6. 2's complement of -48₁₀ is ----
 - (a) 11010000
- (b) 10110000
- (c) 01010000
- (d) 01001111
- 7. Which of the following serve as key memory elements?
 - (a) Switches
- (b) Relays
- (c) Flip flops
- (d) Quartz crystals

Page 2 Code No.: 20493 E

- 8. If the output responds immediately to input signals, then the flip flop is ———
 - (a) transparent
 - (b) positive edge triggered
 - (c) negative edge triggered
 - (d) neutral
- 9. Which of the following flip flop is not used to construct registers?
 - (a) RS
- (b) D
- (c) JK
- (d) T
- 10. Which of the following is used to store a binary number?
 - (a) Array
- (b) Register
- (c) Cell
- (d) Counter

PART B — $(5 \times 5 = 25 \text{ marks})$

Answer ALL questions, choosing either (a) or (b). Each answer should not exceed 250 words.

- 11. (a) (i) Convert the binary 110.001 to a decimal number.
 - (ii) A computer has 2 MB memory. What is the decimal equivalent of 2 MB?

Or

(b) Write a note on ASCII.

Page 3 Code No.: 20493 E

12. (a) Write the consensus theorem.

Or

(b) What is the simplified Boolean equation for the following logic equation?

 $F(A, B, C, D) = \Sigma m(7,9,10,11,12,13,14,15)$

13. (a) Write a note on multiplexer.

Oi

- (b) Perform binary addition (83)10 and (-16)10.
- 14. (a) Write a note on flip flops.

Or

- (b) Write a note on edge triggered D flip flop.
- 15. (a) Explain serial in serial out register.

Or

(b) Explain parallel in parallel out register.

Page 4 Code No.: 20493 E

[P.T.O]

PART C
$$-$$
 (5 \times 8 = 40 marks)

Answer ALL questions, choosing either (a) or (b) Each answer should not exceed 600 words.

16. (a) Tabulate the BCD representation and excess - 3 code for decimal 0 - 9.

Or

- (b) Explain the universal logic gates.
- 17. (a) Construct the truth table for
 - (i) three input NOR gate
 - (ii) three input AND gate.

Or

(b) Write the SOP and POS using Karnaugh map.

$$F(A, B, C, D) = \prod_{d(8,9,11,12,13,15)} M(0, 1.2, 4, 5, 14) +$$

18. (a) Add (-43)₁₀ and (-78)₁₀ in binary form.

Or

- (b) Explain 7 segment decoder.
- 19. (a) Explain edge triggered RS flip flop.

Or

(b) Explain JK master - slave flipflop.

Page 5 Code No.: 20493 E

20. (a) Explain scrial in parallel out register.

Or

(b) Explain universal shift register.

Page 6 Code No.: 20493 E