

## PART A — (10 × 1 = 10 marks)

Answer ALL questions.

Choose the correct answer :

1. Binary coded decimal is a combination of \_\_\_\_\_.
- (a) Two binary digits  
(b) Three binary digits  
(c) Four binary digits  
(d) Five binary digits

7. K-map is used for \_\_\_\_\_.
- (a) logic minimization  
(b) expression maximization  
(c) summing of parity bits  
(d) logic gate creation
8. How many select lines are required for a 1-to-8 demultiplexer?
- (a) 2 (b) 3  
(c) 4 (d) 5
9. A decimal counter has \_\_\_\_\_ states.
- (a) 5 (b) 10  
(c) 15 (d) 20
10. BCD counter is also known as \_\_\_\_\_.
- (a) Parallel counter  
(b) Decade counter  
(c) Synchronous counter  
(d) VLSI counter

2. The excess-3 code for 597 is given by \_\_\_\_\_.
- (a) 100011001010  
(b) 100010100111  
(c) 010110010111  
(d) 010110101101
3. According to boolean law:  $A + 1 = ?$
- (a) 1 (b) A  
(c) 0 (d) A'
4. A \_\_\_\_\_ value is represented by a Boolean expression.
- (a) Positive (b) Recursive  
(c) Negative (d) Boolean
5. In S-R flip-flop, if  $Q = 0$  the output is said to be \_\_\_\_\_.
- (a) Set (b) Reset  
(c) Previous state (d) Current state
6. When both inputs of a J-K flip-flop cycle, the output will \_\_\_\_\_.
- (a) Be invalid (b) Change  
(c) Not change (d) Toggle

## PART B — (5 × 5 = 25 marks)

Answer ALL questions, choosing either (a) or (b).

Each answer should not exceed 250 words.

11. (a) Encode the following decimal number to BCD code.
- (i) 46  
(ii) 327.89  
(iii) 20.305.
- Or
- (b) Find one's complement of the following number
- (i) 10100111  
(ii) 0111.
12. (a) Discuss briefly positive and Negative logic systems.
- Or
- (b) Draw the circuit and working of EX-OR gate with truth table.
13. (a) Describe the working of R-S flip flop with diagram.
- Or
- (b) Describe the working of T-flip flop with a diagram.

14. (a) Explain term  
(i) AND OR realization  
(ii) OR AND realization.

Or

- (b) Briefly explain Multiplexer with diagram.  
15. (a) Differentiate synchronous and Asynchronous Counter. Write a note Binary Counter.

Or

- (b) Explain term  
(i) Linearity and  
(ii) Settling time of a D/A converter.

PART C — (5 × 8 = 40 marks)

Answer ALL questions, choosing either (a) or (b).

Each answer should not exceed 600 words.

16. (a) Determine the decimal number represented by binary number.  
(i) 110101  
(ii) 101101  
(iii) 11111111.

Or

Page 5 Code No. : 10308 E

- (b) ADD Binary numbers  
(i) 1011+1101  
(ii) 1010.1101 + 101.01

Perform the following subtraction

- (i) 1011-0110  
(ii) 1110-1001

17. (a) Write the basic logic gates. Describe the working of OR gate with truth table.

Or

- (b) Explain function of NAND and NOR gates.

18. (a) Explain the operation of JK flipflop with a diagram.

Or

- (b) Briefly Explain working of Monostable Multivibrator with a circuit diagram.

19. (a) Minimize the following boolean function  
 $F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$

Or

- (b) Explain Encoder with a circuit diagram.

Page 6 Code No. : 10308 E

20. (a) Explain Parallel in serial out and Parallel in Parallel out shift registers.

Or

- (b) Explain MOD-5 counter with diagram.

Page 7 Code No. : 10308 E