

2018	III	15	1100	V - 433	(E)
<p style="text-align: center;"><b>ELECTRONICS</b> <b>PAPER - I (C-2)</b></p>					
Time : 3 Hours		3 Pages		Max. Marks : 50	

- Instructions :**
- (1) All questions are compulsory.
  - (2) Draw neat labelled diagrams wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Use of log table is allowed.

1. (A) Select correct alternatives and rewrite the following :

(a) The ripple factor of full wave rectifier is \_\_\_\_\_.

1

(i) 0.48

(ii) 1.21

(iii) 1

(iv) None of these

(b) \_\_\_\_\_ effect is used in LDR.

1

(i) Photoconductive

(ii) Photoconductive

(iii) Photoemissive

(iv) None of these

(c) In IC 741, pin numbers \_\_\_\_\_ are used for offset null adjustment. 1

(i) 4 and 7

(ii) 1 and 5

(iii) 2 and 3

(iv) 4 and 8

(d) In FM, frequency of carrier wave is varied with \_\_\_\_\_ 1

(i) Amplitude of Modulating Signal

(ii) Frequency of Modulating Signal

(iii) Phase of Modulating Signal

(iv) None of these

(B) Answer any two of the following :

(a) In a full wave rectifier centre tapped transformer is used. The secondary voltage is 50V ac. Using ideal diodes calculate the dc load voltage, current rating and PIV rating for the diodes. 3

Given :  $R_L = 47\Omega$

(b) In inverting amplifier  $R_i = 1\text{ K}\Omega$   $R_f = 5\text{ K}\Omega$ . Calculate output voltage if input voltage is 50 mV. 3

(c) Draw functional block diagram of IC 555 and explain. 3

2. (A) Answer any two of the following :

(a) With the help of a diagram explain electrostatic focussing in CRT. 3

(b) Draw and explain functional block diagram of 3 terminal IC regulator. 3

(c) Explain use of IC 555 as astable multivibrator. 3

(B) Attempt any one of the following :

(a) Explain the following parameters of OP AMP :

(i) CMRR

(ii) Virtual Ground

(iii) Open Loop Gain

(iv) Closed Loop Gain 4

(b) With the help of block diagram, explain the working of FAX transceiver. 4

3. (A) Answer any two of the following :

(a) Explain how a CRO displays a waveform. 3

(b) Draw and explain V-I graph of Zener Diode. 3

(c) Explain use of OP-AMP as a subtractor. 3

- (B) Answer **any one** of the following :
- (a) Explain the **working** of LVDT. State its uses. 4
  - (b) Draw the block diagram of pulsed RADAR and explain function of each block. 4
4. (A) Answer **any two** of the following :
- (a) Explain use of front panel control of CRO. (**Any Three**) 3
  - (b) Draw and explain RC filter circuit. State its disadvantages. 3
  - (c) Draw and explain OP-AMP as a non inverting amplifier. 3
- (B) Answer **any one** of the following :
- (a) Draw block diagram of OP-AMP and explain function of each block. 4
  - (b) Compare FM with AM (**Any 8 points**) 4
5. (A) Answer **any two** of the following :
- (a) The spot of a CRO is shifted by 4 cm when 10 volt dc is applied to its vertical input. Find maximum displacement of spot when 8V ac is applied. 3
  - (b) Draw the block diagram of regulated power supply and briefly explain the function of each block. 3
  - (c) Explain why modulation is necessary in communication. 3
- (B) Answer **any one** of the following :
- (a) Define Active and Passive Transducer. Explain the working of variable plate capacitive transducer. 4
  - (b) Draw the circuit diagram of OP-AMP as Schmidt Trigger. With the help of waveforms explain how it converts sine wave to square wave. 4
- OR**
5. (A) Answer **any two** of the following :
- (a) Draw block diagram of DMM and explain function of each block. 3
  - (b) State any three advantages of differential amplifier over RC coupled amplifier. 3
  - (c) Draw Pin diagram of IC 741 and state its applications. 3
- (B) Answer **any one** of the following :
- (a) Explain current limiting in a transistorised series regulator circuit. 4
  - (b) Why networking is necessary in communication systems ? Explain WAN and MAN. 4



2018	III	17	1100	V - 467	(E)
<b>ELECTRONICS</b> <b>PAPER - II (C-2)</b>					
Time : 3 Hours		4 Pages		Max. Marks : 50	

- Instructions :**
- (1) All questions are compulsory.
  - (2) Figures to the right indicate full marks.
  - (3) Draw neat diagrams where necessary.
  - (4) Use of log tables is allowed.

1. (A) Select the correct alternatives and rewrite the following sub-questions :

(a) When one of the input of two input Ex-OR Gate is high, it acts as

a \_\_\_\_\_

1

(i) NOT Gate

(ii) AND Gate

(iii) OR Gate

(iv) NAND Gate

(b) In tri-state logic, the third state is \_\_\_\_\_ state.

1

(i) low impedance

(ii) high impedance

(iii) low

(iv) high

(c) In J-K Flip-flop, when  $J=1$  and  $K=1$ , if \_\_\_\_\_ when clock pulse arrives.

1

(i) Sets

(ii) Resets

(iii) Toggles

(iv) Races

(d) In a counter type analog to digital converters \_\_\_\_\_ comparators comparator are/is used. 1

(i) one

(ii) two

(iii) three

(iv) four

(B) Answer any two of the following :

(a) Convert the following : 3

(i)  $(947)_{16} = (X)_{10}$

(ii)  $(111)_{10} = (X)_2$

(iii)  $(11011)_2 = (X)_{10}$

(b) Explain working of Decimal to BCD encoder using OR gates with truth-table and a neat diagram. 3

(c) How many Flip-flops are required to construct : 3

(i) MOD-15 Counter

(ii) MOD-25 Counter

(iii) MOD-8 Counter

2. (A) Answer any two of the following :

(a) Write a short note on : ASCII Code. 3

(b) Draw a neat logic diagram for given Boolean equation. Write its truth table. 3

$$Y = (A + B) \cdot (\overline{A \cdot B})$$

(c) Explain in brief semiconductor memories used in computer. 3

(B) Answer any one of the following :

(a) Explain operation of Decade counter with logic diagram, truth table and waveforms. 4

(b) Explain the working of weighted resistor type D/A converter with suitable diagram. State its advantages and disadvantages. 4

3. (A) Answer any two of the following :
- (a) Perform subtraction using is complement method of subtraction : 3
    - (i)  $(1011)_2 - (10001)_2$
    - (ii)  $(1011)_2 - (101)_2$
  - (b) Explain the following terms for Digital ICs : 3
    - (i) Noise Margin
    - (ii) Fan Out
    - (iii) Figure of Merit
  - (c) What is a Multiplexer ? Explain 4 : 1 MUX with logic diagram and truth table. 3
- (B) Answer any one of the following :
- (a) Draw the block diagram of a computer and explain function of each block. 4
  - (b) State and prove De Morgan's theorems. 4
4. (A) Answer any two of the following :
- (a) Explain with suitable examples conversion of hexadecimal to decimal number system. 3
  - (b) Explain how basic gates are constructed using NOR gates. 3
  - (c) Explain the working of J-K Flip-flop with logic diagram and truth table. 3
- (B) Attempt any one of the following :
- (a) Implement the following multi-output. 4
 

Combinational logic circuit using 4 line to 16 line decoder/Demux.

$$F_1 = \sum m(1, 3, 4, 6, 8, 10)$$

$$F_2 = \sum m(5, 8, 11, 14)$$

$$F_3 = \sum m(4, 8, 13)$$
  - (b) Draw a block diagram and explain the working of simultaneous A/D converters. State its advantages and disadvantages. 4

5. (A) Answer any two of the following :

- (a) What are Different Number Systems ? Define radix of a number system. Mention it for each of the number system. 3
- (b) Draw the circuit of TTL NAND gate and explain its working with truth table. 3
- (c) Implement the following logic expression using a Multiplexer IC : 3

$$Y = \bar{A} \bar{B} \bar{C} + \bar{A} B \bar{C} + A \bar{B} \bar{C} ABC$$

(B) Answer any one of the following :

- (a) Draw the diagram of 4-bit shift-left register using D Flip-flops and explain its working with waveforms. 4
- (b) Prove the following identities using Boolean laws only : 4
  - (i)  $(A + B)(A + C) = A + BC$
  - (ii)  $ABC + A\bar{B}C + AB\bar{C} = A(B + C)$

OR

5. (A) Answer any two of the following :

- (a) Explain the working of CMOS NAND gate with a neat circuit diagram. 3
- (b) Explain the need of Multiplexing and Demultiplexing. 3
- (c) In a 4-bit R-2R ladder D/A converter find : 3
  - (i) Full scale output voltage.
  - (ii) Analog output voltage for 1011 input.

(Given : Logic '0' = 0V and Logic '1' = +15V)

(B) Answer any one of the following :

- (a) Explain the working of Up-down counter with logic diagram and truth table. 4
- (b) What is a Decoder ? Explain BCD to seven segment decoder/driver with neat logic diagram. 4